



**IL2234**

Digital Systems Design and Verification  
using Hardware Description Languages

**Project Milestone 1**


Combinational Circuits

## Introduction

In this milestone, we will build the first component of our microprocessor: the Arithmetic Logic Unit (ALU). We will design and model the ALU circuit based on the SystemVerilog modelling concepts learned in the class. Additionally, we will develop a simple testbench to test the basic functionality of the ALU.

## Overview

Below is a simple diagram of the ALU

 

The inputs and outputs are described in the table below

Name	Direction	Type	Bitwidth	Description
in_a	Input	logic signed	BW <sup>1</sup>	Operand A
in_b	Input	logic signed	BW <sup>1</sup>	Operand B
opcode	Input	logic	3	Operation code
out	Output	logic signed	BW <sup>1</sup>	Output result
flags	Output	logic signed	3	Flags of the result (overflow, negative, and zero detect)

<sup>1</sup> BW is a configurable parameter that defines the bitwidth of the ALU operands

The ALU behaviour is defined according to the following table.

Opcode	Name	Output	Description
000	ADD	$\text{in\_a} + \text{in\_b}$	Addition
001	SUB	$\text{in\_a} - \text{in\_b}$	Subtraction
010	AND	$\text{in\_a} \text{ AND } \text{in\_b}$	Logic AND
011	OR	$\text{in\_a} \text{ OR } \text{in\_b}$	Logic OR
100	XOR	$\text{in\_a} \text{ XOR } \text{in\_b}$	Logic XOR
101	INC	$\text{in\_a} + 1$	Increment
110	MOVA	$\text{in\_a}$	Passthrough A
111	MOVB	$\text{in\_b}$	Passthrough B

Note that the inputs and outputs for arithmetic operations are in 2's complement format.

The flag output consists of 3 active high flags (overflow, negative, and zero detect) and works as follows:

- **Overflow:** asserted (1) if the result of AND or SUB gives the incorrect sign, i.e., the operation has an overflow. Deasserted (0) otherwise.
- **Negative:** asserted (1) if the result of **any** operation is a negative number. Deasserted (0) otherwise.
- **Zero detect:** asserted (1) if the result of **any** operation is zero. Deasserted (0) otherwise.

The three flags are combined in a 3-bit output as follows:

```
assign flags = {overflow,negative,zero};
```

## Tasks

1. Design the ALU according to the specifications presented earlier. Write your code in System Verilog using **only synthesizable** constructs. Follow the same naming for the signals indicated in the diagrams and tables.
2. Write a testbench that generates inputs for the operands and opcodes; you may use randomisation functions to generate these inputs.



3. Simulate the ALU (DUT) in the testbench and check that the results are correct. Generate the necessary stimuli so all operations are checked, with multiple operands for each operation.

## **Deliverables**

Use GitHub Classroom to submit your RTL and testbench files.

The GitHub Classroom repositories contain a skeleton of the RTL and testbench files for the ALU that you may use for your development.