

Topic 5B

PUNEH Processor



Outline


- ▶ **Computer Hardware**
- ▶ **Computer Software**
- ▶ **Instruction Set Architecture**
- ▶ **PUNEH as a Test-Case Processor**

Outline


- ▶ *Computer Hardware*
- ▶ **Computer Software**
- ▶ **Instruction Set Architecture**
- ▶ **PUNEH as a Test-Case Processor**

Computer Hardware

 - **RTL Design**
 - **Datapath**
 - **Controller**



 opcode
 ir_on_adr
 pc_on_adr
 dbus_on_data
 data_on_bus
 Id_ir
 Id_ac
 Id_pc
 inc_pc
 clr_pc
 pass
 alu_on_dbus
 add




Outline

- ▶ **Computer Hardware**
- ▶ ***Computer Software***
- ▶ **Instruction Set Architecture**
- ▶ **PUNEH as a Test-Case Processor**

Computer Software

- Level of Programming Languages

 

Computer Software

- **High-Level Language**

- Such as C, FORTRAN, or Pascal that enables a programmer to write programs that are more or less independent of a particular type of computer.
- Such languages are considered high-level because they are closer to human languages and further from machine languages.

```
void main()  
{  
    return b*h/2  
};
```

Computer Software

- **Assembly Language**

- Machine language programs are tedious and error-prone to write, and difficult to understand.
- The programmers used a symbolic notation called assembly language.
- Assembly language is easier to use than machine language.

```
Load r1,b  
Load r2,h  
Mul   r1,r2  
Div   r1,#2  
Ret
```


Computer Software

- **Machine Language**

- Machine language is a collection of binary digits or bits
- The computer alphabet is just two letters 0 and 1
- Instructions are binary numbers meaningful for a computer
- The binary notation is referred to as the machine language


00010010010
00101001001
00111011001
0101101001

Outline

- ▶ **Computer Hardware**
- ▶ **Computer Software**
- ▶ ***Instruction Set Architecture***
- ▶ **PUNEH as a Test-Case Processor**

Instruction Set Architecture

 - Instruction set architecture (ISA) is an abstract model of a processor
- Hardware/Software Interface




Outline

- ▶ **Computer Hardware**
- ▶ **Computer Software**
- ▶ **Instruction Set Architecture**
- ▶ ***PUNEH as a Test-Case Processor***

PUNEH as a Test-Case Processor

 - A processor is a digital circuit that performs tasks defined for it in its memory
- Tasks are broken into individual instructions



PUNEH as a Test-Case Processor

- **CPU Specification**

The CPU design begins with the specification of the CPU, including:

1. Number of general-purpose registers
2. Memory organization
 - Whether byte or word addressable.
3. Instruction format
4. Addressing modes
 - direct, indirect, ...

PUNEH as a Test-Case Processor

- **PUNEH CPU Specification**
(**P**rocessor that is **U**seful and **N**ew for **E**ducation of **H**ardware)

1. Number of general-purpose registers


- PC (Program Counter)
- OF (Offset)
- AC (Accumulator)
- IR (Instruction Register)

PUNEH as a Test-Case Processor

- **PUNEH CPU Specification**
(Processor that is Useful and New for Education of Hardware)

 2. Memory organization

- 16-bit address bus
- Capable of addressing 2^{16} locations of memory through its 16-bit address bus (addrbus)
- 16-bit (2 bytes) addressable
- **Write access** to the memory requires 1 clock cycle
- **Read access** to the memory is combinational




PUNEH as a Test-Case Processor

- **PUNEH CPU Specification**
(**P**rocessor that is **U**seful and **N**ew for **E**ducation of **H**ardware)

3. Instruction format

- 16-bit instruction format

 

PUNEH as a Test-Case Processor

- **PUNEH CPU Specification**
(**P**rocessor that is **U**seful and **N**ew for **E**ducation of **H**ardware)

4. Addressing modes

- *Immediate:*

- The operand is specified in the instruction explicitly.
- Instead of address field, an operand field is present that contains the operand.

- Direct
- Indirect




Immediate Addressing Mode

PUNEH as a Test-Case Processor

- **PUNEH CPU Specification**
(**P**rocessor that is **U**seful and **N**ew for **E**ducation of **H**ardware)

 4. Addressing modes

- Immediate:
- *Direct*
 - The address field of the instruction contains the effective address of the operand.
 - Only one reference to memory is required to fetch the operand.
- Indirect



PUNEH as a Test-Case Processor


- **PUNEH CPU Specification**
(Processor that is Useful and New for Education of Hardware)

4. Addressing modes

- Immediate:
- Direct

- *Indirect*

 - The address field of the instruction specifies the address of memory location that contains the effective address of the operand.
- Two references to memory are required to fetch the operand.



PUNEH as a Test-Case Processor

- PUNEH has a total of 26 instructions
- Three addressing modes for address
 - X_m indicating immediate addressing mode
 - X_a indicating direct addressing mode
 - X_n indicating indirect addressing mode
- General Purpose Instructions
 - Data Transfer Instructions
 - Logical Instructions
 - Arithmetic Instructions
 - Shift Instructions
 - Control Transfer Instructions
 - Flag Control Instructions




Instruction Type	Opcode	Instruction	Description
Full Address Instr.	0000	LDm	Load Accumulator Immediate
	0001	LDa	Load Accumulator Addressed
	0010	LDn	Load Accumulator Indirect
	0011	STa	Store Accumulator Addressed
	0100	STn	Store Accumulator Indirect
	0101	INa	Increment memory Address
	0110	ANm	AND Accumulator Immediate
	0111	ANa	AND Accumulator Addressed
	1000	ADm	Add Accumulator Immediate
	1001	ADa	Add Accumulator Addressed
	1010	ADn	Add Accumulator Indirect
	1011	MLa	Multiply Accumulator Addressed
	1100	JMa	Jump Addressed (unconditional)
	1101	JMn	Jump Indirect
	1110	JSR	Jump Sub-routine

PUNEH as a Test-Case Processor



- General Purpose Instructions
 - Data Transfer Instructions
 - Logical Instructions
 - Arithmetic Instructions
 - Shift Instructions
 - Control Transfer Instructions
 - Flag Control Instructions

Instruction Type	Opcode		Instruction	Description
No Address Instr.	1111	0000	00000000	LPO Load PC to Offset register
			00000001	LOP Load Offset register to PC
			00000010	ACZ Accumulator Zero
			00000011	ACN Accumulator NOT
			00000100	ACI Accumulator Increment
		0001		LOm Load Offset register Immediate
		0010		SRA Shift Right Arithmetic
		0011		SRL Shift Right Logical
		0100		SLL Shift Left Logical
		0101		SKP_{Z,N,C,V} Skip Zero, Negative, Carry, Overflow (obs, exp)
		0110		SET_{Z,N,C,V} Set Zero, Negative, Carry, Overflow (enb, val)

 


PUNEH as a Test-Case Processor

- RTL Datapath Design

  

Controller Design

 

PUNEH as a Test-Case Processor


Opcode	Instruction	Description
0000	LDm	Load Accumulator Immediate

Exec1

LDm :

```
SE4bits = 1;
selIMM_AC = 1;
ldAC = 1;
```
 
```
INC1 = 1;  
selINC_PC = 1;  
ldPC = 1;
```



PUNEH as a Test-Case Processor


Opcode	Instruction	Description
0001	LDa	Load Accumulator Addressed

Exec1

LDa :

```
conOF = 1;
selIR_ADR = 1;
readMEM = 1;
selMEM_AC = 1;
ldAC = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor

Opcode	Instruction	Description
0010	LDn	Load Accumulator Indirect

Exec1

LDn :


```
conOF = 1;
selIR_ADR = 1;
readMEM = 1;
selMEM_IN = 1;
ldIN = 1;
```

Exec2

LDn :

```
selIN_ADR = 1;
readMEM = 1;
selMEM_AC = 1;
ldAC = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor


Opcode	Instruction	Description
0011	STa	Store Accumulator Addressed

Exec1

STa :

```
conOF = 1;
selIR_ADR = 1;
selAC_MEM = 1;
seldataBus = 1;
writeMEM = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor

Opcode	Instruction	Description
0110	ANm	AND Accumulator Immediate


Exec1

ANm :

```
SE4bits = 1;
selIMM_LGU = 1;
AND = 1;
selLGU_AC = 1;
ldAC = 1;
```

```
selLGU_SR = 1;
ldSR = 4'b1100;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor


Opcode	Instruction	Description
1001	ADa	Add Accumulator Addressed

Exec1

ADa :

```

 conOF = 1;
selIR_ADR = 1;
readMEM = 1;
selMEM_LGU = 1;
selMO_ARU = 1;
ADD = 1;
selARU_AC = 1;
ldAC = 1;
selARU_SR = 1;
ldSR = 4'b1111;
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
    
```



PUNEH as a Test-Case Processor


Opcode	Instruction	Description
1101	JMn	Jump Indirect

Exec1

JMn :

```

 conOF = 1;
selIR_ADR = 1;
readMEM = 1;
selMEM_PC = 1;
ldPC = 1;
    
```



PUNEH as a Test-Case Processor


Opcode			Instruction	Description
1111	0000	00000000	LPO	Load PC to Offset register

Exec1

LPO :

```
selPC_OF = 1;
ldOF = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor


Opcode			Instruction	Description
1111	0000	00000100	ACI	Accumulator Increment

Exec1

ACI :

```
sel1_ARU = 1;
ADD = 1;
sel1_ARU_AC = 1;
ldAC = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor


Opcode	Instruction	Description
1111	0011	SRL Shift Right Logical

Exec1

SRL :

```
SE12bits = 1;
selIMM_LGU = 1;
SHF = 2'b01;
selLGU_AC = 1;
ldAC = 1;
```
 
```
INC1 = 1;
selINC_PC = 1;
ldPC = 1;
```



PUNEH as a Test-Case Processor

Opcode	Instruction	Description
1111	0101	SKP _{Z,N,C,V} Skip Zero, Negative, Carry, Overflow (obs, exp)

Exec1

SKP :

```
if (enSKP)
```


```
    INC2 = 1;
```

```
else
```

```
    INC1 = 1;
```

```
selINC_PC = 1;
```


```
ldPC = 1;
```

 

PUNEH as a Test-Case Processor

- **Multi-Cycle Implementation**

 
- Datapath Design
- Controller Design
- **Datapath Description**
- **Controller Description**
- **The Complete Design**



PUNEH as a Test-Case Processor

- Datapath
- LGU, ARU, Mux2to1, Mux4to1

```
45 // Arithmetic Units
46 LGU LGU1 (AC_MEM, MO, LGU_AC, AND, NOT, SHF, Z1, N1);
47 ARU ARU1 (AC_MEM, MO_ARU, ARU_AC, ADD, MUL, Z2, N2, C, V);
48
49 // MUXes
50 Mux2to1 #(16) mux1 (16'd1, MO, sel1_ARU, selMO_ARU, MO_ARU);
51 Mux2to1 #(16) mux2 (IMM AC, MEM AC, selIMM LGU, selMEM LGU, MO);
52 Mux4to1 #(16) mux3 (IMM_AC, MEM_AC, ARU_AC, LGU_AC, selIMM_AC,
53 selMEM_AC, selARU_AC, selLGU_AC, toAC);
54 Mux2to1 #(4) mux4 (PC_MEM[15:12], IMM_AC[3:0], selPC_OF, selIMM_OF, toOF);
55 Mux4to1 #(16) mux5 (INC_PC, MEM_AC, IMM_AC, 16'bz, selINC_PC,
56 selMEM_PC, selIMM_PC, 1'bz, toPC);
57 Mux2to1 #(16) mux6 (INC2 out, MEM AC, selINC_IN, selMEM_IN, toIN);
58 Mux4to1 #(16) mux7 (IN_MEM, INC_PC, AC_MEM, 16'bz, selIN_MEM,
59 selPC_MEM, selAC_MEM, 1'bz, toBuff);
60 Mux4to1 #(16) mux8 (IN_MEM, IMM_AC, PC_MEM, 16'bz, selIN_ADR,
61 selIR_ADR, selPC_ADR, 1'bz, addrBus);
62 Mux2to1 #(2) mux9 (2'd2, 2'd1, INC2, INC1, toINC);
63 Mux4to1 #(4) mux10 (IRout[3:0], {Z1, N1, 2'bz}, {Z2, N2, C, V}, 4'bz, selSET_SR,
64 selLGU_SR, selARU_SR, 1'bz, toSR);
65
66
```

 

PUNEH as a Test-Case Processor

- Datapath
- Registers, IMM, INC, TriBuff

```
// Registers
```

```
Register #(16) AC (clk, rst, toAC, AC_MEM, ldAC, zeroAC);
```

```
Register #(16) IR (clk, rst, MEM_AC, IRout, ldIR, 1'b0);
```

```
Register #(16) PC (clk, rst, toPC, PC_MEM, ldPC, 1'b0);
```

```
Register #(16) IN (clk, rst, toIN, IN_MEM, ldIN, 1'b0);
```

```
Register #(4) OF (clk, rst, toOF, OFout, ldOF, 1'b0);
```

```
Register #(1) SR_Z (clk, rst, toSR[3], w[3], ldSR[3], 1'b0);
```

```
Register #(1) SR_N (clk, rst, toSR[2], w[2], ldSR[2], 1'b0);
```

```
Register #(1) SR_C (clk, rst, toSR[1], w[1], ldSR[1], 1'b0);
```

```
Register #(1) SR_V (clk, rst, toSR[0], w[0], ldSR[0], 1'b0);
```


```
// The Other Components
```

```
IMM IMM1 (IRout[11:0], OFout, IMM_AC, conOF, SE12bits, SE4bits, LSB0E);
```

```
INC INC_1 (PC_MEM, toINC, INC_PC);
```

```
INC INC_2 (MEM_AC, 2'd1, INC2_out);
```
 
```
Tristate TriBuff (toBuff, dataBus, seldataBus);
```




PUNEH as a Test-Case Processor

- Datapath
- Flag registers
- Flag assignments

```
73 Register #(1) SR_Z (clk, rst, toSR[3], w[3], ldSR[3], 1'b0);
74 Register #(1) SR_N (clk, rst, toSR[2], w[2], ldSR[2], 1'b0);
75 Register #(1) SR_C (clk, rst, toSR[1], w[1], ldSR[1], 1'b0);
76 Register #(1) SR_V (clk, rst, toSR[0], w[0], ldSR[0], 1'b0);
77
```

```
84 // Flags
85 assign exp = IRout[3:0];
86
87 assign w[4] = w[0] ^ exp[0];
88 assign w[5] = w[1] ^ exp[1];
89 assign w[6] = w[2] ^ exp[2];
90 assign w[7] = w[3] ^ exp[3];
91
92 assign obs = IRout[7:4];
93
94 assign w[8] = w[4] & obs[0];
95 assign w[9] = w[5] & obs[1];
96 assign w[10] = w[6] & obs[2];
97 assign w[11] = w[7] & obs[3];
98
99 assign enSKP = w[8] | w[9] | w[10] | w[11];
100
101 assign MEM_AC = dataBus;
102
103 endmodule
```

 


PUNEH as a Test-Case Processor

- **ARU (Arithmetic Unit)**

```
module ARU (
    input logic signed [15:0] in0, in1,
    output logic signed [15:0] out,
    input logic ADD, MUL,
    output logic Z, N, C, V
);
    always_comb begin
        C = 1'b0;
        out = 16'b0;

        if (ADD)
            {C, out} = in0 + in1;
        else if (MUL)
            out = in0[7:0] * in1[7:0];
    end

    assign Z = ~|out;
    assign N = out[15];
    assign V = (in0[15] & in1[15] & ~out[15]) || (~in0[15] & ~in1[15] & out[15]);
endmodule
```

 

PUNEH as a Test-Case Processor

- LGU (Logic Unit)

```


module LGU (
    input  logic signed [15:0] in0, in1,
    output logic signed [15:0] out,
    input  logic AND, NOT,
    input  logic [1:0] SHF,
    output logic Z, N
);

    always_comb begin
        out = 16'b0;

        if (AND == 1'b1)
            out = in0 & in1;
        else if (NOT == 1'b1)
            out = ~in0;
        else if (SHF == 2'b00)
            out = in0 >>> in1;
        else if (SHF == 2'b01)
            out = in0 >> in1;
        else if (SHF == 2'b10)
            out = in0 << in1;
        else
            out = 16'b0;
    end

    assign Z = ~|out;
    assign N = out[15];
endmodule

```

 


PUNEH as a Test-Case Processor

- Registers

```

 module Register #(parameter N) (
    input  logic clk, rst,
    input  logic [N-1:0] in,
    output logic [N-1:0] out,
    input  logic ld, clr
);
    always_ff @(posedge clk, posedge rst) begin
        if (rst)
            out <= 'b0;
        else if (clr)
            out <= 'b0;
        else if (ld)
            out <= in;
        end
    endmodule
    
```



PUNEH as a Test-Case Processor


- IMM (Immediate)

```

module IMM (
    input logic [11:0] in0,
    input logic [3:0] in1,
    output logic [15:0] out,
    input logic conOF, SE12bits, SE4bits, LSB0E
);
    always_comb begin
        out = 16'b0;

        if (conOF)
            out = {in1, in0};
        else if (LSB0E)
            out = {in1, 12'd0};
        else if (SE12bits)
            out = {{12{in0[3]}} , in0[3:0]};
        else if (SE4bits)
            out = {{4{in0[11]}} , in0};
        else
            out = 16'b0;
    end
endmodule


```

 

PUNEH as a Test-Case Processor

- INC (Incrementer)
 
```
module INC (  
    input logic [15:0] in,  
    input logic [1:0] inc_val,  
    output logic [15:0] out  
);  
    assign out = in + inc_val;  
endmodule
```



PUNEH as a Test-Case Processor

• Mux2to1

```

module Mux2to1 #(parameter N) (
    input logic [N-1:0] in0, in1,
    input logic sel0, sel1,
    output logic [N-1:0] out
);

always_comb begin
    out = 16'b0;

    if (sel0)
        out = in0;
    else if (sel1)
        out = in1;
    end

endmodule

```

• Mux4to1

```


module Mux4to1 #(parameter N) (
    input logic [N-1:0] in0, in1, in2, in3,
    input logic sel0, sel1, sel2, sel3,
    output logic [N-1:0] out
);

always_comb begin
    out = 16'b0;

    if (sel0)
        out = in0;
    else if (sel1)
        out = in1;
    else if (sel2)
        out = in2;
    else if (sel3)
        out = in3;
    end

endmodule


```

 

PUNEH as a Test-Case Processor

- Tristate
 
```
module Tristate (  
    input logic [15:0] in,  
    output logic [15:0] out,  
    input logic oe  
);  
    assign out = oe ? in : 16'bz;  
endmodule
```



PUNEH as a Test-Case Processor

- Controller

```
typedef enum logic [1:0] {
    fetch = 2'b00,
    exec1 = 2'b01,
    exec2 = 2'b10
} state_t;

state_t pstate, nstate;

typedef enum logic [3:0] {
    LDm      = 4'b0000,
    LDa      = 4'b0001,
    LDn      = 4'b0010,
    STa      = 4'b0011,
    STn      = 4'b0100,
    INa      = 4'b0101,
    ANm      = 4'b0110,
    ANa      = 4'b0111,
    ADm      = 4'b1000,
    ADa      = 4'b1001,
    ADn      = 4'b1010,
    MLa      = 4'b1011,
    JMa      = 4'b1100,
    JMn      = 4'b1101,
    JSR      = 4'b1110,
    INST15   = 4'b1111
} instr_type1;
```

```
typedef enum logic [3:0] {
    TYPE3    = 4'b0000,
    LOm      = 4'b0001,
    SRA      = 4'b0010,
    SRL      = 4'b0011,
    SLL      = 4'b0100,
    SKP      = 4'b0101,
    SET      = 4'b0110
} instr_type2;

typedef enum logic [7:0] {
    LPO      = 8'b00000000,
    LOP      = 8'b00000001,
    ACZ      = 8'b00000010,
    ACN      = 8'b00000011,
    ACI      = 8'b00000100
} instr_type3;
```

PUNEH as a Test-Case Processor

- Huffman Model

- Register part of controller

```
always_ff @(posedge clk, posedge rst) begin
    if (rst)
        pstate <= fetch;
    else
        pstate <= nstate;
end
```


- **Output transition**
- **Fetch, Exec1**

- **Output transition**
- **Exec1**

[illegible]


PUNEH as a Test-Case Processor

- **Output transition**
- **Exec1**

```

144 Ada : begin
145     conOF = 1; selIR_ADR = 1; readMEM = 1;
146     selMEM_LGU = 1; selMO_ARU = 1; ADD = 1;
147     selARU_AC = 1; ldAC = 1;
148     selARU_SR = 1; ldSR = 4'b1111;
149     INC1 = 1; selINC_PC = 1; ldPC = 1;
150 end
151 ADn : begin
152     conOF = 1; selIR_ADR = 1; readMEM = 1;
153     selMEM_IN = 1; ldIN = 1;
154 end
155 MLa : begin
156     conOF = 1; selIR_ADR = 1; readMEM = 1;
157     selMEM_LGU = 1; selMO_ARU = 1; MUL = 1;
158     selARU_AC = 1; ldAC = 1;
159     selARU_SR = 1; ldSR = 4'b1000;
160     INC1 = 1; selINC_PC = 1; ldPC = 1;
161 end
162 JMa : begin
163     conOF = 1; selIMM_PC = 1; ldPC = 1;
164 end
165 JMn : begin
166     conOF = 1; selIR_ADR = 1; readMEM = 1;
167     selMEM_PC = 1; ldPC = 1;
168 end
169 JSR : begin
170     conOF = 1; selIR_ADR = 1; INC1 = 1;
171     selPC_MEM = 1; seldataBus = 1;
172     writeMEM = 1; selIMM_PC = 1; ldPC = 1;
173 end

```

 


PUNEH as a Test-Case Processor

- **Output transition**
- **Exec1**

```

174 INST15 : begin case (inst[11:8])
175     TYPE1 : begin case (inst[7:0])
176         LPO : begin
177             selPC_OF = 1;  ldOF  = 1;
178             INC1 = 1;  selINC_PC = 1;  ldPC = 1;
179         end
180         LOP : begin
181             LSB0E = 1;  selIMM_PC = 1;  ldPC = 1;
182         end
183         ACZ : begin
184             zeroAC = 1;
185             selLGU_SR = 1;  ldSR = 4'b1100;
186             INC1 = 1;  selINC_PC = 1;  ldPC = 1;
187         end
188         ACN : begin
189             NOT = 1;  selLGU_AC = 1;  ldAC = 1;
190             selLGU_SR = 1;  ldSR = 4'b1100;
191             INC1 = 1;  selINC_PC = 1;  ldPC = 1;
192         end
193         ACI : begin
194             sel1_ARU = 1;  ADD = 1;
195             selARU_AC = 1;  ldAC = 1;
196             INC1 = 1;  selINC_PC = 1;  ldPC = 1;
197         end
198         default : begin
199             INC1 = 1;  selINC_PC = 1;  ldPC = 1;
200         end
201     end
202 endcase
203 end

```

 


PUNEH as a Test-Case Processor

- **Output transition**
- **Exec1**

```

203 | LOm : begin
204 |     SE12bits = 1; selIMM_OF = 1; ldOF = 1;
205 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
206 | end
207 | SRA : begin
208 |     SE12bits = 1; selIMM_LGU = 1; SHF = 2'b00;
209 |     selLGU_AC = 1; ldAC = 1;
210 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
211 | end
212 | SRL : begin
213 |     SE12bits = 1; selIMM_LGU = 1; SHF = 2'b01;
214 |     selLGU_AC = 1; ldAC = 1;
215 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
216 | end
217 | SLL : begin
218 |     SE12bits = 1; selIMM_LGU = 1; SHF = 2'b10;
219 |     selLGU_AC = 1; ldAC = 1;
220 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
221 | end
222 | SKP : begin
223 |     if (enSKP) INC2 = 1;
224 |     else INC1 = 1;
225 |     selINC_PC = 1; ldPC = 1;
226 | end
227 | SET : begin
228 |     selSET_SR = 1; ldSR = inst[7:4];
229 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
230 | end
231 | default : begin
232 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
233 | end
234 | endcase
235 | end
236 | default : begin
237 |     INC1 = 1; selINC_PC = 1; ldPC = 1;
238 | end
239 | endcase
240 | end

```

 


PUNEH as a Test-Case Processor

- Output transition
- Exec1, Exec2

```

240
241
242
243
244
245
246
247
248
249
250
251
252
253
254
255
256
257
258
259
260
261
262
263
264
265
266
267
268
269
end
exec2 : begin case (inst[15:12])
  LDn : begin
    selIN_ADR = 1; readMEM = 1;
    selMEM_AC = 1; ldAC = 1;
    INC1 = 1; selINC_PC = 1; ldPC = 1;
  end
  STn : begin
    selIN_ADR = 1; selAC_MEM = 1;
    seldataBus = 1; writeMEM = 1;
    INC1 = 1; selINC_PC = 1; ldPC = 1;
  end
  INa : begin
    conOF = 1; selIR_ADR = 1; selIN_MEM = 1;
    seldataBus = 1; writeMEM = 1;
    INC1 = 1; selINC_PC = 1; ldPC = 1;
  end
  ADn : begin
    selIN_ADR = 1; readMEM = 1; selMEM_LGU = 1;
    selMO_ARU = 1; ADD = 1; selARU_AC = 1; ldAC = 1;
    selARU_SR = 1; ldSR = 4'b1111;
    INC1 = 1; selINC_PC = 1; ldPC = 1;
  end
  JSR : begin
    INC1 = 1; selINC_PC = 1; ldPC = 1;
  end
endcase
end
endcase
end

```

 

PUNEH as a Test-Case Processor

```

always_comb begin
    nstate = fetch;
    case (pstate)
        fetch :
            nstate = exec1;
        exec1 : begin case (inst[15:12])
            LDm :    nstate = fetch;
            LDa :    nstate = fetch;
            LDn :    nstate = exec2;
            STa :    nstate = fetch;
            STn :    nstate = exec2;
            INa :    nstate = exec2;
            ANm :    nstate = fetch;
            ANa :    nstate = fetch;
            ADm :    nstate = fetch;
            ADa :    nstate = fetch;
            ADn :    nstate = exec2;
            MLa :    nstate = fetch;
            JMa :    nstate = fetch;
            JMn :    nstate = fetch;
            JSR :    nstate = exec2;
            INST15 : nstate = fetch;
            default: nstate = fetch;
        endcase
    end
    exec2 : begin
        nstate = fetch ;
    end
    default :
        nstate = fetch;
    endcase
end

```

PUNEH as a Test-Case Processor

- Top Module
- Datapath
- Controller

```
module TopLevel (
    input logic clk, rst,
    inout logic [15:0] dataBus,
    output logic writeMEM, readMEM,
    output logic [15:0] addrBus
);
    logic [15:0] inst;
    logic [3:0] ldSR;
    logic [1:0] SHF;
    logic enSKP, ldIR, ldOF, ldPC, ldIN, ldAC, zeroAC, seldataBus, selPC_OF,
        selIMM_OF, selMEM_IN, selIMM_LGU, selMEM_LGU, sel1_ARU, selMO_ARU,
        selINC_PC, selMEM_PC, selIMM_PC, selIN_ADR, selIR_ADR, selPC_ADR,
        selAC_MEM, selIMM_AC, selMEM_AC, selARU_AC, selLGU_AC, conOF,
        SE12bits, SE4bits, AND, NOT, ADD, MUL, selSET_SR, selINC_IN,
        INC1, INC2, selARU_SR, selLGU_SR, selIN_MEM, selPC_MEM, LSB0E;


    Datapath DP (clk, rst, AND, NOT, ADD, MUL, sel1_ARU, selMO_ARU, selIMM_LGU,
        selMEM_LGU, ldAC, zeroAC, selIMM_AC, selMEM_AC, selARU_AC,
        selLGU_AC, ldPC, selINC_PC, selMEM_PC, selIMM_PC, ldIN,
        selINC_IN, selMEM_IN, conOF, SE12bits, SE4bits, ldIR, ldOF,
        selPC_OF, selIMM_OF, selIN_ADR, selPC_ADR, selAC_MEM, selIR_ADR,
        seldataBus, INC1, INC2, selSET_SR, selLGU_SR, selARU_SR, selIN_MEM, selPC_MEM, LSB0E,
        dataBus, SHF, ldSR, addrBus, enSKP);

    Controller CU (clk, rst, enSKP, inst, ldIR, ldOF, ldPC, ldIN, ldAC, zeroAC, seldataBus,
        selPC_OF, selIMM_OF, selINC_IN, selMEM_IN, selIMM_LGU, selMEM_LGU,
        sel1_ARU, selMO_ARU, selINC_PC, selMEM_PC, selIMM_PC, selIN_ADR,
        selIR_ADR, selPC_ADR, selAC_MEM, selIMM_AC, selMEM_AC, selARU_AC,
        selLGU_AC, conOF, SE12bits, SE4bits, AND, NOT, ADD, MUL,
        readMEM, writeMEM, selSET_SR, INC1, INC2, selARU_SR, selLGU_SR, selIN_MEM, selPC_MEM, LSB0E,
        SHF, ldSR);
endmodule
```


PUNEH as a Test-Case Processor

- **Programming in PUNEH**

 - **Instruction-by-instruction testing**
- **Fibonacci sequence**
 - A series of numbers where each number is the sum of the two preceding ones
 - Starting with 0 and 1, resulting in 0, 1, 1, 2, 3, 5, 8, 13, ...
 - $F(n) = F(n-1) + F(n-2)$ for $n > 1$, with $F(0) = 0$ and $F(1) = 1$



PUNEH as a Test-Case Processor

- Programming in PUNEH
- Fibonacci
 - C program

F(10)=0,1,1,2,3, 5, 8, 13, 21, 34

• Assembly Code

```
1  #include<stdio.h>
2  int main()
3  {
4      int n1=0,n2=1,n3,i,number;
5      printf("Enter the number of elements: ");
6      scanf("%d",&number);
7      printf("\n%d %d",n1,n2);
8      for(i=2;i<number;++i)
9      {
10         n3=n1+n2;
11         printf(" %d",n3);
12         n1=n2;
13         n2=n3;
14     }
15     return 0;
16 }
```

```
14 //*****
15 // File content description:
16 // Fibonacci assembly code for the PUNEH processor
17 //*****
18
19 #define n 10
20 #define a0 111
21 #define a1 112
22 #define t 113
23 #define cntr 114
24 #define pointer 115
25
26 mem[0] = FA(LDm, -n+2);
27 mem[1] = FA(STa, cntr);
28 mem[2] = FA(LDm, 128);
29 mem[3] = FA(STa, pointer);
30 mem[4] = FA(LDm, 0);
31 mem[5] = FA(STa, a0);
32 mem[6] = FA(STn, pointer);
33 mem[7] = FA(INa, pointer);
34 mem[8] = FA(LDm, 1);
35 mem[9] = FA(STa, a1);
36 mem[10] = FA(STn, pointer);
37 mem[11] = FA(INa, pointer);
38 // loop:
39 mem[12] = FA(LDa, a0);
40 mem[13] = FA(ADa, a1);
41 mem[14] = FA(STa, t);
42 mem[15] = FA(STn, pointer);
43 mem[17] = FA(LDa, a1);
44 mem[18] = FA(STa, a0);
45 mem[19] = FA(LDa, t);
46 mem[20] = FA(STa, a1);
47 mem[21] = FA(INa, pointer);
48 mem[22] = FA(INa, cntr);
49 mem[23] = FA(LDa, cntr);
50 mem[24] = FA(ADm, 0);
51 mem[25] = NA(SKp, 0x8, 0x8);
52 mem[26] = FA(JMa, 12);
```

// results will store in mem[128] to mem[128+abs(n)]

• Binary Code

```
14 //*****
15 // File content description:
16 // Fibonacci binary code for the PUNEH processor
17 //*****
18
19 00001111111111000
20 0011000001110010
21 0000000010000000
22 0011000001110011
23 0000000000000000
24 0011000001101111
25 0100000001110011
26 0101000001110011
27 0000000000000001
28 0011000001110000
29 0100000001110011
30 0101000001110011
31 0001000001101111
32 1001000001110000
33 0011000001110001
34 0100000001110011
35 0001000001110000
36 0011000001101111
37 0001000001110001
38 0011000001110000
39 0101000001110011
40 0101000001110010
41 0001000001110010
42 1000000000000000
43 1111010110001000
44 1100000000001100
```

PUNEH as a Test-Case Processor

• Simulation Result

