
 


Topic 5

RTL Methodology

 



Outline

5- RTL Methodology


Basic Design Flow

Serial Adder

Divider Circuit


Sequential Multiplier

Exponential Accelerator

 

Basic Design Flow

- **Step 1:** Understanding the problem
- **Step 2:** Find a hardware-oriented algorithm for solving the problem
- **Step 3:** Datapath - Controller partitioning
 - Place all the required combinational and sequential components in the datapath
 - Decide on the bussing structure interconnecting sequential and combinational components
 - Decide what control signals components and buses of a datapath require
 - Considering RTL timing design control FSM(s) responsible for issuing datapath and external control signals
- **Step 4:** Implement the design in SystemVerilog

 

Outline



5- RTL Methodology

Basic Design Flow

Serial Adder


Divider Circuit

Sequential Multiplier

  


Finite State Machine

Serial Adder


 


 - After a complete pulse on start, data on a_{in} and b_{in} are serially added
- After 8 clock cycles, the sum result, $Parout$, is ready
- Ready signal is issued and will be asserted until the next start





Finite State Machine

Serial Adder

  




Finite State Machine

Serial Adder - Datapath

  




Finite State Machine

Serial Adder - Controller

   

Finite State Machine

Serial Adder - Controller

   

Outline

5- RTL Methodology


Basic Design Flow

Serial Adder

Divider Circuit

Sequential Multiplier

Exponential Accelerator

 


Divider Circuit

- Let's exercise this design flow with a simple divider circuit

Step 1.

Find what the problem wants you to solve

 

Divider Circuit

Step 2.

Find an algorithm for the solution

- **Step 2.1:** Subtract the divisor from the dividend.
- **Step 2.2:** Keep subtracting until you cannot subtract anymore
- **Step 2.3:** keep a count of how many subtractions you can do


Step 2.2 gives you the remainder
Step 2.3 gives you the quotient

$$\begin{array}{r} 26 \div 7 = 3r5 \\ \hline 26 - 7 = 19 \text{ (1)} \\ 19 - 7 = 12 \text{ (2)} \\ 12 - 7 = 5 \text{ (3)} \\ 5 - 7 = -2 \text{ (X)} \end{array}$$


Divider Circuit

Step 3. Datapath - Controller Partitioning

 - **Subtract** the divisor from the dividend (WHAT: Datapath)



 
- **Keep** subtracting the divisor (WHAT: Datapath)




Divider Circuit

Step 3. Datapath - Controller Partitioning

A Better
Choice

 

 
- Count how many times you subtracted the divisor (WHAT : Datapath)



Divider Circuit



Step 3. Datapath- Controller Partitioning

Datapath

 

Divider Circuit

  
Step 3. Datapath- Controller Partitioning



Divider Circuit


Step 3. Datapath - Controller Partitioning

 - Repeat until you cannot subtract anymore (WHEN : Controller)
 - Stop when subtraction result's sign-bit is one.



Divider Circuit

 Step 3. Datapath- Controller Partitioning





Divider Circuit

Step 3.

Datapath- Controller Partitioning

Controller

  

Outline

5- RTL Methodology



Basic Design Flow

Serial Adder

Divider Circuit



Sequential Multiplier

Exponential Accelerator

  

Sequential Multiplier

Shift-Add Multiplier

  



B: 1 0 1 1 0 1 1 0
A: 1 0 0 1 0 1 0 0

0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0
0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0

1 1 0 1 0 0 1 0 0 1 1 1 0 0 0




Sequential Multiplier

Shift-Add Multiplier

  

Sequential Multiplier

Shift-Add Multiplier

  
 


Put A in a shift-register, always observe its right-most bit, and after every calculation, we move it one place to the right, making its next bit accessible.

For the partial products, instead of writing one and the next one to its left, we move the partial product to the right as we are writing it.



Sequential Multiplier

Shift-Add Multiplier

  


Sequential Multiplier

Shift-Add Multiplier

  

Sequential Multiplier

Shift-Add Multiplier

 

$t = 3$ $0011 + 0000 \rightarrow 0001\textcircled{1}$

0 0 0 1

1 0 1 1

1 1 0 1

$t = 4$ $0001 + 1101 \rightarrow 0111\textcircled{0}$

0 1 1 1 0 1 0 1



1 1 0 1

Result

The least significant 4 bits of the multiplication result become available in A and the most-significant bits in P.



Sequential Multiplier

Shift-Add Multiplier

  




Sequential Multiplier

Shift-Add Multiplier (Datapath)

  

Sequential Multiplier

Shift-Add Multiplier (Controller)

   

Sequential Multiplier

Shift-Add Multiplier

(Datapath SystemVerilog)

```


module multiplier_DP (
    input logic clk, rst,
    input logic loadA, loadB, loadP, shiftA, InitP, Bsel,
    input logic [3:0] ABus, BBus,
    output logic [7:0] ResultBus,
    output logic A0
);

    logic [3:0] Areg, Breg, Preg;
    logic [3:0] B_AND;
    logic [4:0] AddBus;

    always_ff @(posedge clk or posedge rst) begin
        if (rst)
            Breg <= 4'b0;
        else if (loadB)
            Breg <= BBus;
    end

    always_ff @(posedge clk or posedge rst) begin
        if (rst)
            Preg <= 4'b0;
        else if (InitP)
            Preg <= 4'b0;
        else if (loadP)
            Preg <= AddBus[4:1];
    end
end

```

 

```

always_ff @(posedge clk or posedge rst) begin
    if (rst)
        Areg <= 4'b0;
    else if (loadA)
        Areg <= ABus;
    else if (shiftA)
        Areg <= {AddBus[0], Areg[3:1]};
end


assign B_AND = Bsel ? Breg : 4'b0;
assign AddBus = B_AND + Preg;
assign ResultBus = {Preg, Areg};
assign A0 = Areg[0];

endmodule



```


Sequential Multiplier

 Shift-Add Multiplier (Controller SystemVerilog)



```
module multiplier_CU (  
    input logic      clk,  
    input logic      rst,  
    input logic      start,  
    input logic      A0,  
    output logic      loadA, shiftA, loadB, loadP, InitP, Bsel, ready  
);  
  
    typedef enum logic [1:0] {  
        Idle   = 2'b00,  
        Init   = 2'b01,  
        load   = 2'b10,  
        shift  = 2'b11  
    } state_t;  
  
    logic Co;  
    logic Init_counter, Inc_counter;  
    logic [1:0] Count;  
    state_t pstate, nstate;
```

  

Sequential Multiplier

Shift-Add Multiplier

(Controller SystemVerilog)

```

always_comb begin
    nstate = Idle;
    {loadA, shiftA, loadB, loadP, InitP, Bsel, ready} = 7'b0;
    {Init_counter, Inc_counter} = 2'b00;

    case (pstate)
        Idle: begin
            nstate = start ? Init : Idle;
            ready = 1'b1;
        end
        Init: begin
            nstate = start ? Init : load;
            Init_counter = 1'b1;
            InitP = 1'b1;
        end
        load: begin
            nstate = shift;
            loadA = 1'b1;
            loadB = 1'b1;
        end
        shift: begin
            nstate = Co ? Idle : shift;
            loadP = 1'b1;
            shiftA = 1'b1;
            Inc_counter = 1'b1;
            Bsel = A0;
        end
        default: begin
            nstate = Idle;
        end
    endcase
end

```



```

always_ff @(posedge clk or posedge rst) begin
    if (rst)
        pstate <= Idle;
    else
        pstate <= nstate;
    end

    always_ff @(posedge clk or posedge rst) begin
        if (rst)
            Count <= 2'b00;
        else begin
            if (Init_counter)
                Count <= 2'b00;
            else if (Inc_counter)
                Count <= Count + 1;
            end
        end

        assign Co = &Count;
    end
endmodule

```

 
 


Sequential Multiplier

Shift-Add Multiplier (Top-level SystemVerilog)

```
module multiplier_top (  
    input  logic      clk, rst,  
    input  logic      start,  
    input  logic [3:0] ABus, BBus,  
    output logic [7:0] ResultBus,  
    output logic      ready  
);  
  
    logic A0;  
    logic loadA, shiftA, loadB, loadP, InitP, Bsel;  
  
    multiplier_DP dp (  
        .clk(clk),  
        .rst(rst),  
        .loadA(loadA),  
        .loadB(loadB),  
        .loadP(loadP),  
        .shiftA(shiftA),  
        .InitP(InitP),  
        .Bsel(Bsel),  
        .ABus (ABus),  
        .BBus (BBus),  
        .ResultBus (ResultBus),  
        .A0 (A0)  
    );  
endmodule
```
  
```
multiplier_CU cu (  
    .clk(clk),  
    .rst(rst),  
    .start(start),  
    .A0 (A0),  
    .loadA(loadA),  
    .shiftA(shiftA),  
    .loadB(loadB),  
    .loadP(loadP),  
    .InitP(InitP),  
    .Bsel(Bsel),  
    .ready(ready)  
);  
endmodule
```



Outline

5- RTL Methodology



Basic Design Flow

Serial Adder

Divider Circuit

Sequential Multiplier

Exponential Accelerator

  

Exponential Circuit

$$e^x = 1 + \frac{x^1}{1!} + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \frac{x^5}{5!} + \frac{x^6}{6!} + \frac{x^7}{7!} + \dots$$


Input X is 16 bit-fraction $0 \leq X < 1$

$$e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!}$$

```
r = 1; // 1 for result
t = 1; // 1 for term
for( k = 1; k < n; k++ )
{
    t = t * x * ( 1 / k );
    r = r + t;
}
```


 
```
r = 1; // 1 for result
t = 1; // 1 for term
for( k = 1; k < n; k++ )
{
    t = t * x
    t = t * ( 1 / k );
    r = r + t;
}
```




Exponential Circuit

$$e^x = 1 + \frac{x^1}{1!} + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \frac{x^5}{5!} + \frac{x^6}{6!} + \frac{x^7}{7!} + \dots$$

Input X is 16 bit-fraction $0 \leq X < 1$
 
```
r = 1; // 1 for result
t = 1; // 1 for term
for( k = 1; k < n; k++ )
{
    t = t * x
    t = t * ( 1 / k );
    r = r + t;
}
```




Exponential Circuit

Datapath

```

 r = 1; // 1 for result
t = 1; // 1 for term
for( k = 1; k < n; k++ )
{
    t = t × x
    t = t × ( 1 / k );
    r = r + t;
}
    
```



Exponential Circuit

Datapath (SystemVerilog)

```


module exp_DP (
    input logic      clk,
    input logic      rst_n,
    input logic      ldx, sel,
    input logic      initt, ldt,
    input logic      initr, ldr,
    input logic      zc, enc,
    input logic [15:0] x,
    output logic      co,
    output logic [17:0] result
);

    logic [15:0] data, m_out, term_in;
    logic [15:0] term_out, xr;
    logic [17:0] res_in;
    logic [2:0]  addr;

    register #(.BIT_WIDTH(16)) regx    (.clk(clk), .rst_n(rst_n), .init0(), .init1(), .load(ldx),
                                         .in_value(x), .out_value(xr));
    counter  #(.BIT_WIDTH(3))  counter (.clk(clk), .rst_n(rst_n), .init0(zc), .enable(enc),
                                         .count(addr), .co(co));
    LUT      #(.BIT_WIDTH(16)) lut      (.addr(addr), .data(data));
    mux2to1  #(.BIT_WIDTH(16)) mux      (.a(xr), .b(data), .sel(sel), .out_value(m_out));
    multiplier #(.BIT_WIDTH(16)) mult   (.a(m_out), .b(term_out), .out_value(term_in));
    register #(.BIT_WIDTH(16),
               .INIT_VALUE(16'hFFFF)) rterm (.clk(clk), .rst_n(rst_n), .init0(), .init1(initt), .load(ldt),
                                              .in_value(term_in), .out_value(term_out));
    adder     #(.BIT_WIDTH(18)) add      (.a({2'b00, term_out}), .b(result), .sum(res_in), .c_out());
    register #(.BIT_WIDTH(18),
               .INIT_VALUE(18'h10000)) rres (.clk(clk), .rst_n(rst_n), .init0(), .init1(initr), .load(ldr),
                                              .in_value(res_in), .out_value(result));


endmodule

```

 

Exponential Circuit

Datapath (SystemVerilog)


 


LUT

```
module LUT (  
    input  logic [2:0]  addr,  
    output logic [15:0] data);  
  
    always_comb begin  
        data = 16'h0000;  
  
        case(addr)  
            0: data = 16'hFFFF;  
            1: data = 16'h8000; // 1/2  
            2: data = 16'h5555; // 1/3  
            3: data = 16'h4000; // 1/4  
            4: data = 16'h3333; // 1/5  
            5: data = 16'h2AAA; // 1/6  
            6: data = 16'h2492; // 1/7  
            7: data = 16'h2000; // 1/8  
        endcase  
    end  
endmodule
```


Exponential Circuit

Controller

  

Exponential Circuit

Controller (SystemVerilog)

 


```

module exp_CU (
    input logic clk,
    input logic rst_n,
    input logic start,
    input logic co,
    output logic done,
    output logic ldx,
    output logic initt, ldt,
    output logic initr, ldr,
    output logic zc, enc, sel
);

typedef enum logic [2:0] {
    IDLE      = 3'd0,
    INIT      = 3'd1,
    LOAD      = 3'd2,
    MULT1     = 3'd3,
    MULT2     = 3'd4,
    ADD       = 3'd5
} state_t;

 state_t present_state, next_state;
    
```





Exponential Circuit Controller (SystemVerilog)

```
always_ff @(posedge clk or negedge rst_n) begin
    if (!rst_n)
        present_state <= IDLE;
    else
        present_state <= next_state;
end
```

```
always_comb begin
    next_state = IDLE;

      case (present_state)
        IDLE: next_state = (!start) ? IDLE : INIT;
        INIT: next_state = (start) ? INIT : LOAD;
        LOAD: next_state = MULT1;
        MULT1: next_state = MULT2;
        MULT2: next_state = ADD;
        ADD: next_state = (co) ? IDLE : MULT1;
        default: next_state = IDLE;
    endcase
end
```



Exponential Circuit Controller (SystemVerilog)

```
always_comb begin
    done    = 1'b0;
    ldx     = 1'b0; sel = 1'b0;
    initt   = 1'b0; ldt = 1'b0;
    initr   = 1'b0; ldr = 1'b0;
    zc      = 1'b0; enc = 1'b0;
end
```

```
case (present_state)
  IDLE: begin
    done = 1'b1;
  end
```

```
  INIT: begin
    zc    = 1'b1;
    initr = 1'b1;
    initt = 1'b1;
  end
```



```
  LOAD: begin
    ldx = 1'b1;
  end
```

```
  MULT1: begin
    sel = 1'b0;
    ldt = 1'b1;
  end
```

```
  MULT2: begin
    sel = 1'b1;
    ldt = 1'b1;
  end
end
```



```
  ADD: begin
    ldr = 1'b1;
    enc = 1'b1;
  end

    default: begin
    done    = 1'b0;
    ldx     = 1'b0; sel    = 1'b0;
    initt   = 1'b0; ldt    = 1'b0;
    initr   = 1'b0; ldr    = 1'b0;
    zc      = 1'b0; enc    = 1'b0;
  end
endcase
```



Exponential Circuit

Top Level

  

Exponential Circuit



Top Level

```
module exp_top (  
    input logic clk,  
    input logic rst_n,  
    input logic start,  
    input logic [15:0] x,  
    output logic done,  
    output logic [1:0] intpart,  
    output logic [15:0] fracpart  
);  
  
    logic ldx, sel;  
    logic initt, ldt;  
    logic initr, ldr;  
    logic zc, enc, co;
```

```
exp_DP datapath (  
    .clk      (clk),  
    .rst_n    (rst_n),  
    .ldx      (ldx),  
    .initt    (initt),  
    .ldt      (ldt),  
    .initr    (initr),  
    .ldr      (ldr),  
    .zc       (zc),  
    .enc      (enc),  
    .sel      (sel),  
    .x        (x),  
    .co       (co),  
    .result   ({intpart, fracpart})  
);
```

```
exp_CU control (  
    .clk      (clk),  
    .rst_n    (rst_n),  
    .start    (start),  
    .co       (co),  
    .done     (done),  
    .ldx      (ldx),  
    .initt    (initt),  
    .ldt      (ldt),  
    .initr    (initr),  
    .ldr      (ldr),  
    .zc       (zc),  
    .enc      (enc),  
    .sel      (sel)  
);
```

```
endmodule
```

  

Conclusion

We have covered these topics:

- Basic RTL design flow
- Serial Adder
- Sequential Divider
- Sequential Multiplier
- Exponential Accelerator

